
Tyler Elvis, 4/2/24, ENRG 108

Table of Contents

Final Project	1
Objectives	1
Code	1

Final Project

```
clc, clear
format short, format compact
```

Objectives

```
% Find the voltage and current through each component in the system.
% Use the current loop directions shown in the schematic.
% Check to determine if the resistor R5 will fail.
% Display the results using appropriate Matlab display commands.
```

Code

```
% all values of the resistors
R1 = 100;
R2 = 500;
R3 = 500;
R4 = 750;
R5 = 500;
R6 = 200;
R7 = 1000;
R8 = 250;
R9 = 1000;
R10 = 750;
R11 = 500;
R12 = 500;
R13 = 500;
R14 = 500;

% all values of the ERG source in volts
V1 = 9;
V2 = 5;
V3 = 15;

% Values of all ending terms of the equations
V = [0; V1; V1; 0; 0; V2; V3];

% All Resistors * current loop matrices
Rcoef = [(R1+R3+R2), -R3, -R2, 0, 0, 0, 0;
          0, R2, 0, 0, 0, 0, 0;
          0, 0, R2, 0, 0, 0, 0;
          0, 0, 0, R4, 0, 0, 0;
          0, 0, 0, 0, R5, 0, 0;
          0, 0, 0, 0, 0, R6, 0;
          0, 0, 0, 0, 0, 0, R7];
```

```
-R2,      (R2+R4+R9), -R4, -R9, 0, 0, 0;
      -R3, -R5, (R3+R5+R7), -R7, 0, 0, 0;
-R7, -R8, -R6, (R7+R8+R6), 0, 0, 0;
      -R9, -R10, -R6, 0, (R9+R10+R6), 0, 0;
      -R4, -R10, 0, 0, 0, (R1+R4+R10+R13), 0;
      -R8, -R5, 0, 0, 0, 0, (R12+R14+R8+R5)];

% left div to find all I values of each loop
I = Rcoef\V;

% Takes each of the answers from I and turns into own variable
I1 = I(1);
I2 = I(2);
I3 = I(3);
I4 = I(4);
I5 = I(5);
I6 = I(6);
I7 = I(7);

% outside loop check
% the equations of R * I values
Check_ = (R11+R13), (R12+R14), R1, 0, 0, 0, 0;

% outside loop check end terms of equations
V_Check = [V2+V3];

% use left div to find the total value
Check = round(Check_\V_Check);

% if else statement for the value above, so if its below or equal to
% zero is very good but if its above zero its bad, if its above but
% close to zero it still checks out.
if Check <=0
    fprintf('The Voltage going through the outside loop is %4.2f
and checks out \n', Check);
else
    fprintf('The Voltage going through the outside loop is %4.2f
and does not check out', Check);
end

format bank

% Currents going through resistor
C_R1 = I1;
C_R2 = I1 - I2;
C_R3 = I1 - I3;
C_R4 = I2 - I4;
C_R5 = I3 - I5;
C_R6 = I4 - I5 - I6;
C_R7 = I3 - I4 - I7;
C_R8 = I4 - I7;
C_R9 = I2 - I5;
C_R10 = I5 - I6;
```

```
C_R11 = I6;
C_R12 = I7;
C_R13 = I6;
C_R14 = I7;

% Voltage running through resistor
V_R1 = R1 * C_R1;
V_R2 = R2 * C_R2;
V_R3 = R3 * C_R3;
V_R4 = R4 * C_R4;
V_R5 = R5 * C_R5;
V_R6 = R6 * C_R6;
V_R7 = R7 * C_R7;
V_R8 = R8 * C_R8;
V_R9 = R9 * C_R9;
V_R10 = R10 * C_R10;
V_R11 = R11 * C_R11;
V_R12 = R12 * C_R12;
V_R13 = R13 * C_R13;
V_R14 = R14 * C_R14;

% Resistor Check
if C_R5 < 10.0
    fprintf("\n \n R5 meets the requirement \n \n")
else
    fprintf("\n \n R5 does not meet requirement \n \n")
end

% getting all of the data nice for table
Resistor = ["R1"; "R2"; "R3"; "R4"; "R5"; "R6"; "R7"; "R8"; "R9";
"R10"; "R11"; "R12"; "R13"; "R14"];
Ohms = [R1; R2; R3; R4; R5; R6; R7; R8; R9; R10; R11; R12; R13; R14];
Voltage = [C_R1; C_R2; C_R3; C_R4; C_R5; C_R6; C_R7; C_R8; C_R9; C_R10;
C_R11; C_R12; C_R13; C_R14];
Current = [ V_R1; V_R2; V_R3; V_R4; V_R5; V_R6; V_R7; V_R8;
V_R9; V_R10; V_R11; V_R12; V_R13; V_R14];

circuit_analysis = table(Resistor, Ohms, Voltage, Current)

Check_ =
    1000
ans =
    1000
R1 =
    100
ans =
     0
ans =
     0
ans =
     0
The Voltage going through the outside loop is 0.00 and checks out
```

R5 meets the requirment

circuit_analysis =

14×4 table

<i>Ressistor</i>	<i>Ohms</i>	<i>Votlage</i>	<i>Current</i>
<i>"R1 "</i>	<i>100.00</i>	<i>0.08</i>	<i>7.57</i>
<i>"R2 "</i>	<i>500.00</i>	<i>-0.01</i>	<i>-3.78</i>
<i>"R3 "</i>	<i>500.00</i>	<i>-0.01</i>	<i>-3.78</i>
<i>"R4 "</i>	<i>750.00</i>	<i>0.01</i>	<i>3.91</i>
<i>"R5 "</i>	<i>500.00</i>	<i>0.00</i>	<i>1.94</i>
<i>"R6 "</i>	<i>200.00</i>	<i>-0.06</i>	<i>-12.09</i>
<i>"R7 "</i>	<i>1000.00</i>	<i>-0.04</i>	<i>-37.94</i>
<i>"R8 "</i>	<i>250.00</i>	<i>0.03</i>	<i>8.71</i>
<i>"R9 "</i>	<i>1000.00</i>	<i>0.00</i>	<i>3.88</i>
<i>"R10 "</i>	<i>750.00</i>	<i>0.02</i>	<i>15.16</i>
<i>"R11 "</i>	<i>500.00</i>	<i>0.06</i>	<i>29.56</i>
<i>"R12 "</i>	<i>500.00</i>	<i>0.04</i>	<i>21.58</i>
<i>"R13 "</i>	<i>500.00</i>	<i>0.06</i>	<i>29.56</i>
<i>"R14 "</i>	<i>500.00</i>	<i>0.04</i>	<i>21.58</i>

Published with MATLAB® R2023b